

Single Cycle Processor Design

COE 301

Computer Organization

Dr. Muhamed Mudawar

College of Computer Sciences and Engineering

King Fahd University of Petroleum and Minerals

Presentation Outline

❖ **Designing a Processor: Step-by-Step**

❖ Datapath Components and Clocking

❖ Assembling an Adequate Datapath

❖ Controlling the Execution of Instructions


❖ Main, ALU, and PC Control

Designing a Processor: Step-by-Step

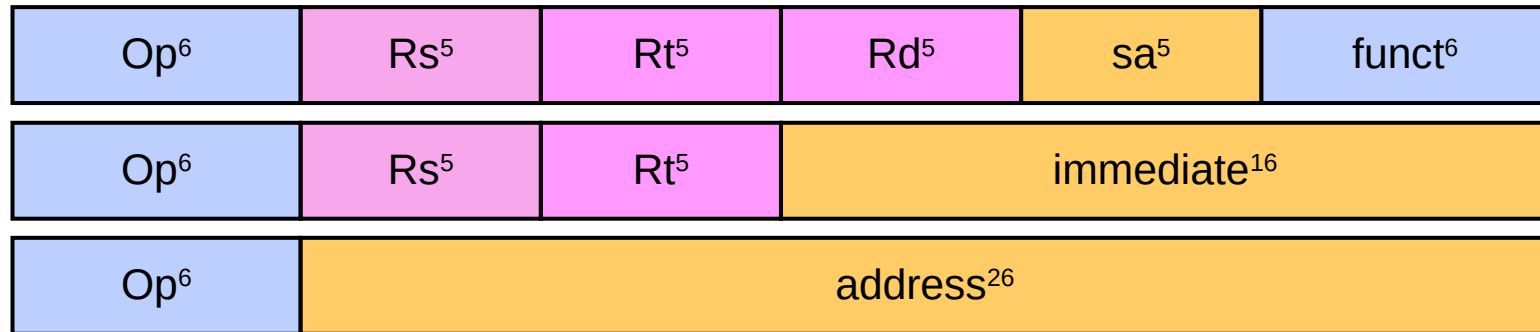1. Analyze instruction set => **datapath requirements**
 - ◇ The meaning of each instruction is given by the **register transfers**
 - ◇ Datapath must include storage elements for ISA registers
 - ◇ Datapath must support each register transfer
2. Select **datapath components** and **clocking methodology**
3. Assemble **datapath** meeting the requirements
4. Analyze implementation of **each instruction**
 - ◇ Determine the setting of **control signals** for register transfer
5. Assemble the **control logic**

Review of MIPS Instruction Formats

- ❖ All instructions are **32-bit wide**
- ❖ Three instruction formats: **R-type**, **I-type**, and **J-type**



- ◇ Op⁶: 6-bit opcode of the instruction
- ◇ Rs⁵, Rt⁵, Rd⁵: 5-bit source and destination register numbers
- ◇ sa⁵: 5-bit shift amount used by shift instructions
- ◇ funct⁶: 6-bit function field for R-type instructions
- ◇ immediate¹⁶: 16-bit immediate constant or PC-relative offset
- ◇ address²⁶: 26-bit target address of the jump instruction

MIPS Subset of Instructions

- ❖ Only a subset of the MIPS instructions is considered
 - ◇ ALU instructions (R-type): **add, sub, and, or, xor, slt**
 - ◇ Immediate instructions (I-type): **addi, slti, andi, ori, xori**
 - ◇ Load and Store (I-type): **lw, sw**
 - ◇ Branch (I-type): **beq, bne**
 - ◇ Jump (J-type): **j**
- ❖ This subset does not include all the integer instructions
- ❖ But sufficient to illustrate design of datapath and control
- ❖ Concepts used to implement the MIPS subset are used to construct a broad spectrum of computers

Details of the MIPS Subset

Instruction		Meaning	Format					
add	rd, rs, rt	addition	$op^6 = 0$	rs^5	rt^5	rd^5	0	0x20
sub	rd, rs, rt	subtraction	$op^6 = 0$	rs^5	rt^5	rd^5	0	0x22
and	rd, rs, rt	bitwise and	$op^6 = 0$	rs^5	rt^5	rd^5	0	0x24
or	rd, rs, rt	bitwise or	$op^6 = 0$	rs^5	rt^5	rd^5	0	0x25
xor	rd, rs, rt	exclusive or	$op^6 = 0$	rs^5	rt^5	rd^5	0	0x26
slt	rd, rs, rt	set on less than	$op^6 = 0$	rs^5	rt^5	rd^5	0	0x2a
addi	rt, rs, imm ¹⁶	add immediate	0x08	rs^5	rt^5	imm ¹⁶		
slti	rt, rs, imm ¹⁶	slt immediate	0x0a	rs^5	rt^5	imm ¹⁶		
andi	rt, rs, imm ¹⁶	and immediate	0x0c	rs^5	rt^5	imm ¹⁶		
ori	rt, rs, imm ¹⁶	or immediate	0x0d	rs^5	rt^5	imm ¹⁶		
xori	rt, imm ¹⁶	xor immediate	0x0e	rs^5	rt^5	imm ¹⁶		
lw	rt, imm ¹⁶ (rs)	load word	0x23	rs^5	rt^5	imm ¹⁶		
sw	rt, imm ¹⁶ (rs)	store word	0x2b	rs^5	rt^5	imm ¹⁶		
beq offset ¹⁶	rs, rt,	branch if equal	0x04	rs^5	rt^5	offset ¹⁶		
bne offset ¹⁶	rs, rt,	branch not equal	0x05	rs^5	rt^5	offset ¹⁶		
j address ²⁶		jump	0x02	address ²⁶				

Single Cycle Processor Design

CSE 301 – Computer Organization © Muhamed Mudawar

Slide 6

Register Transfer Level (RTL)

- ❖ RTL is a description of data flow between registers
- ❖ RTL gives a **meaning** to the instructions
- ❖ All instructions are fetched from memory at address PC

Instruction RTL Description

ADD	$\text{Reg(rd)} \leftarrow \text{Reg(rs)} + \text{Reg(rt)}; \text{PC} \leftarrow \text{PC} + 4$
SUB	$\text{Reg(rd)} \leftarrow \text{Reg(rs)} - \text{Reg(rt)}; \text{PC} \leftarrow \text{PC} + 4$
ORI	$\text{Reg(rt)} \leftarrow \text{Reg(rs)} \mid \text{zero_ext}(\text{imm}^{16}); \text{PC} \leftarrow \text{PC} + 4$
LW	$\text{Reg(rt)} \leftarrow \text{MEM}[\text{Reg(rs)} + \text{sign_ext}(\text{imm}^{16})]; \text{PC} \leftarrow \text{PC} + 4$
SW	$\text{MEM}[\text{Reg(rs)} + \text{sign_ext}(\text{imm}^{16})] \leftarrow \text{Reg(rt)}; \text{PC} \leftarrow \text{PC} + 4$
BEQ	$\text{if } (\text{Reg(rs)} == \text{Reg(rt)})$ $\text{PC} \leftarrow \text{PC} + 4 + 4 \times \text{sign_ext}(\text{offset}^{16})$ $\text{else } \text{PC} \leftarrow \text{PC} + 4$

Instruction Fetch/Execute

❖ R-type

Fetch instruction: $\text{Instruction} \leftarrow \text{MEM}[\text{PC}]$
Fetch operands: $\text{data1} \leftarrow \text{Reg}(\text{rs}), \text{data2} \leftarrow \text{Reg}(\text{rt})$
Execute operation: $\text{ALU_result} \leftarrow \text{func}(\text{data1}, \text{data2})$
Write ALU result: $\text{Reg}(\text{rd}) \leftarrow \text{ALU_result}$
Next PC address: $\text{PC} \leftarrow \text{PC} + 4$

❖ I-type

Fetch instruction: $\text{Instruction} \leftarrow \text{MEM}[\text{PC}]$
Fetch operands: $\text{data1} \leftarrow \text{Reg}(\text{rs}), \text{data2} \leftarrow \text{Extend}(\text{imm}^{16})$
Execute operation: $\text{ALU_result} \leftarrow \text{op}(\text{data1}, \text{data2})$
Write ALU result: $\text{Reg}(\text{rt}) \leftarrow \text{ALU_result}$
Next PC address: $\text{PC} \leftarrow \text{PC} + 4$

❖ BEQ

Fetch instruction: $\text{Instruction} \leftarrow \text{MEM}[\text{PC}]$
Fetch operands: $\text{data1} \leftarrow \text{Reg}(\text{rs}), \text{data2} \leftarrow \text{Reg}(\text{rt})$
Equality: $\text{zero} \leftarrow \text{subtract}(\text{data1}, \text{data2})$
Branch: $\text{if (zero)} \quad \text{PC} \leftarrow \text{PC} + 4 + 4 \times \text{sign_ext}(\text{offset}^{16})$
 $\text{else} \quad \text{PC} \leftarrow \text{PC} + 4$

Instruction Fetch/Execute – cont'd

❖ LW

Fetch instruction: $\text{Instruction} \leftarrow \text{MEM}[\text{PC}]$
Fetch base register: $\text{base} \leftarrow \text{Reg}(\text{rs})$
Calculate address: $\text{address} \leftarrow \text{base} + \text{sign_extend}(\text{imm}^{16})$
Read memory: $\text{data} \leftarrow \text{MEM}[\text{address}]$
Write register Rt: $\text{Reg}(\text{rt}) \leftarrow \text{data}$
Next PC address: $\text{PC} \leftarrow \text{PC} + 4$

❖ SW

Fetch instruction: $\text{Instruction} \leftarrow \text{MEM}[\text{PC}]$
Fetch registers: $\text{base} \leftarrow \text{Reg}(\text{rs}), \text{data} \leftarrow \text{Reg}(\text{rt})$
Calculate address: $\text{address} \leftarrow \text{base} + \text{sign_extend}(\text{imm}^{16})$
Write memory: $\text{MEM}[\text{address}] \leftarrow \text{data}$
Next PC address: $\text{PC} \leftarrow \text{PC} + 4$

❖ Jump

Fetch instruction: $\text{Instruction} \leftarrow \text{MEM}[\text{PC}]$
Target PC address: $\text{target} \leftarrow \text{PC}[31:28] \parallel \text{address}^{26} \parallel \text{'00'}$
Jump: $\text{PC} \leftarrow \text{target}$

concatenation



Requirements of the Instruction Set

❖ Memory

- ❖ **Instruction memory** where instructions are stored
- ❖ **Data memory** where data is stored

❖ Registers

- ❖ **31 × 32-bit general purpose registers**, R0 is always zero
- ❖ Read source register Rs
- ❖ Read source register Rt
- ❖ Write destination register Rt or Rd

❖ Program counter **PC register** and **Adder** to increment PC

❖ Sign and Zero **extender** for immediate constant

❖ **ALU** for executing instructions


Next . . .

- ❖ Designing a Processor: Step-by-Step
- ❖ **Datapath Components and Clocking**
- ❖ Assembling an Adequate Datapath
- ❖ Controlling the Execution of Instructions
- ❖ Main, ALU, and PC Control

Components of the Datapath


❖ Combinational Elements

 - ◇ ALU, Adder
- ◇ Immediate extender
- ◇ Multiplexers



❖ Storage Elements

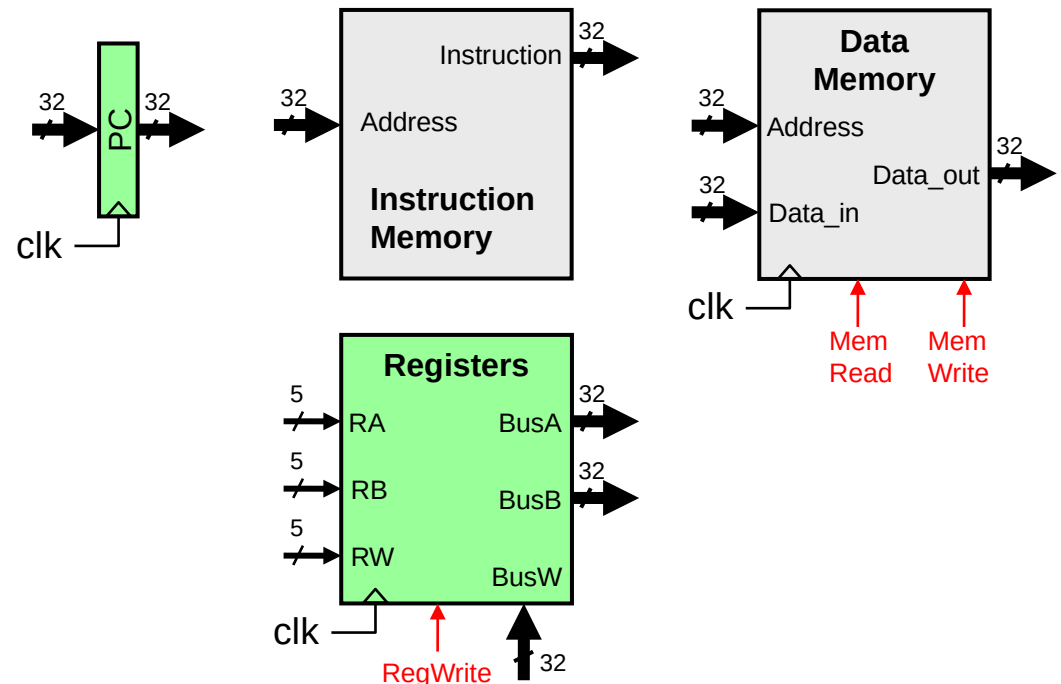- ◇ Instruction memory
- ◇ Data memory
- ◇ PC register
- ◇ Register file



❖ Clocking methodology

- ◇ Timing of writes

Register Element

❖ Register

- ◇ Similar to the D-type Flip-Flop


❖ n-bit input and output

❖ Write Enable (WE):

- ◇ Enable / disable writing of register
- ◇ Negated (0): Data_Out will not change
- ◇ Asserted (1): Data_Out will become Data_In **after clock edge**

❖ Edge triggered Clocking

 - ◇ Register output is modified at **clock edge**




MIPS Register File

- ❖ Register File consists of 31×32 -bit registers
 - ◇ **BusA** and **BusB**: 32-bit output busses for reading 2 registers
 - ◇ **BusW**: 32-bit input bus for writing a register when **RegWrite** is 1
 - ◇ Two registers read and one written in a cycle


- ❖ Registers are selected by:
 - ◇ **RA** selects register to be **read** on **BusA**
 - ◇ **RB** selects register to be **read** on **BusB**
 - ◇ **RW** selects the register to be **written**

- ❖ Clock input

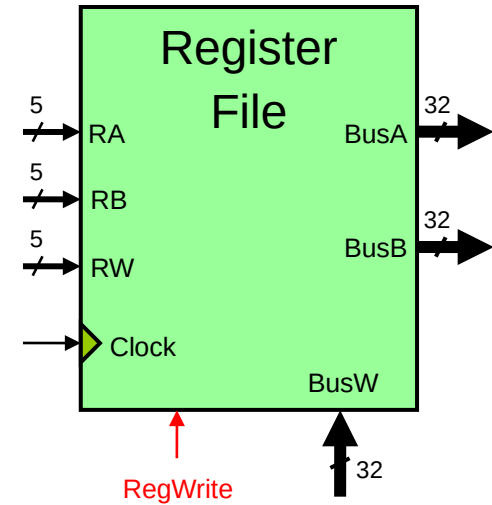- ◇ The clock input is **used ONLY during write** operation
- ◇ During read, register file behaves as a **combinational logic** block
 - RA or RB valid => BusA or BusB valid after **access time**



Details of the Register File

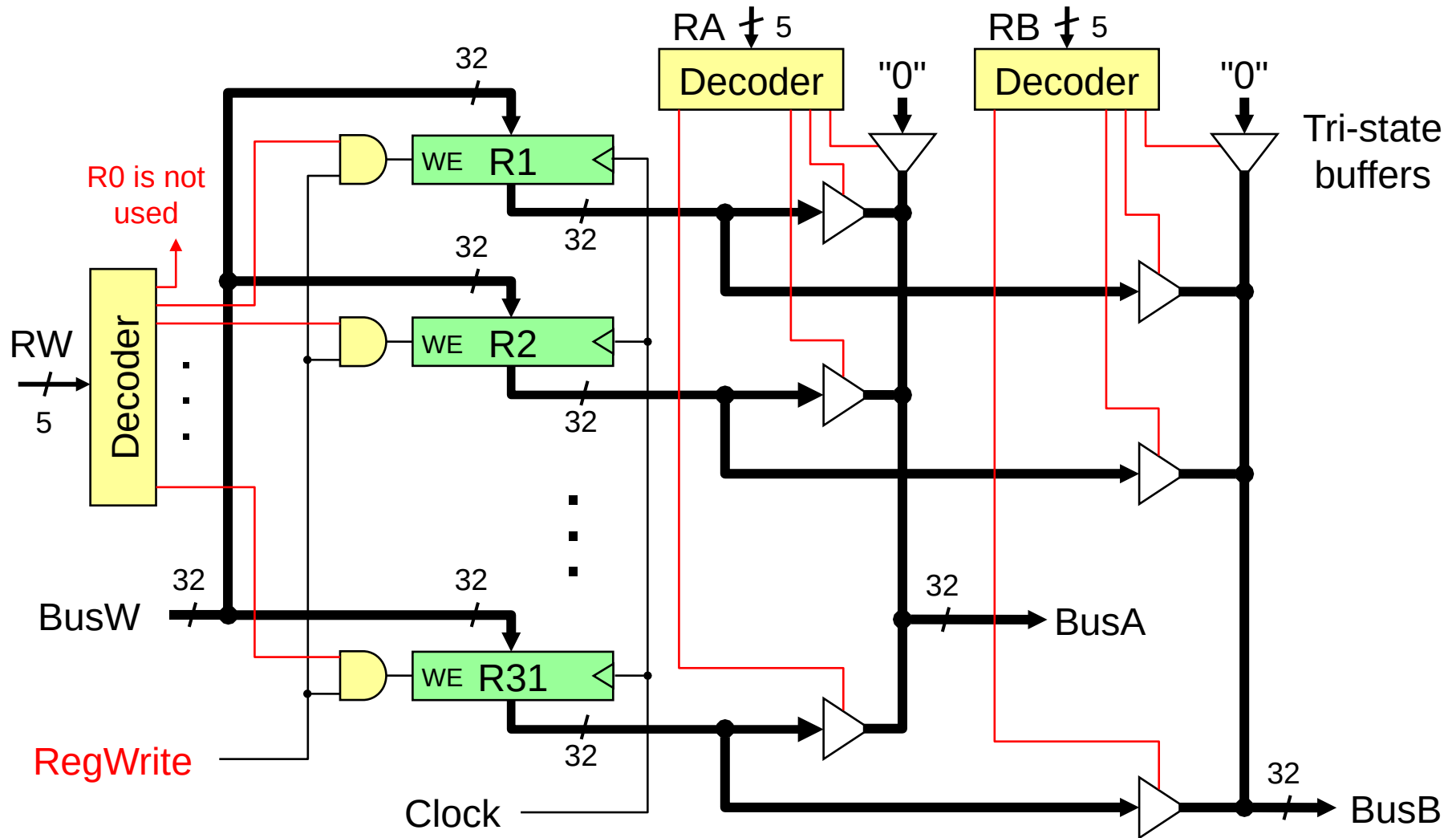

Tri-State Buffers

- ❖ Allow multiple sources to drive a single bus

- ❖ Two Inputs:


 - ◇ Data_in

 - ◇ **Enable** (to enable output)


- ❖ One Output: Data_out

 - ◇ If (**Enable**) Data_out = Data_in

 
 - else Data_out = **High Impedance** state (output is disconnected)



 - ❖ Tri-state buffers can be used to build multiplexors




Building a Multifunction ALU

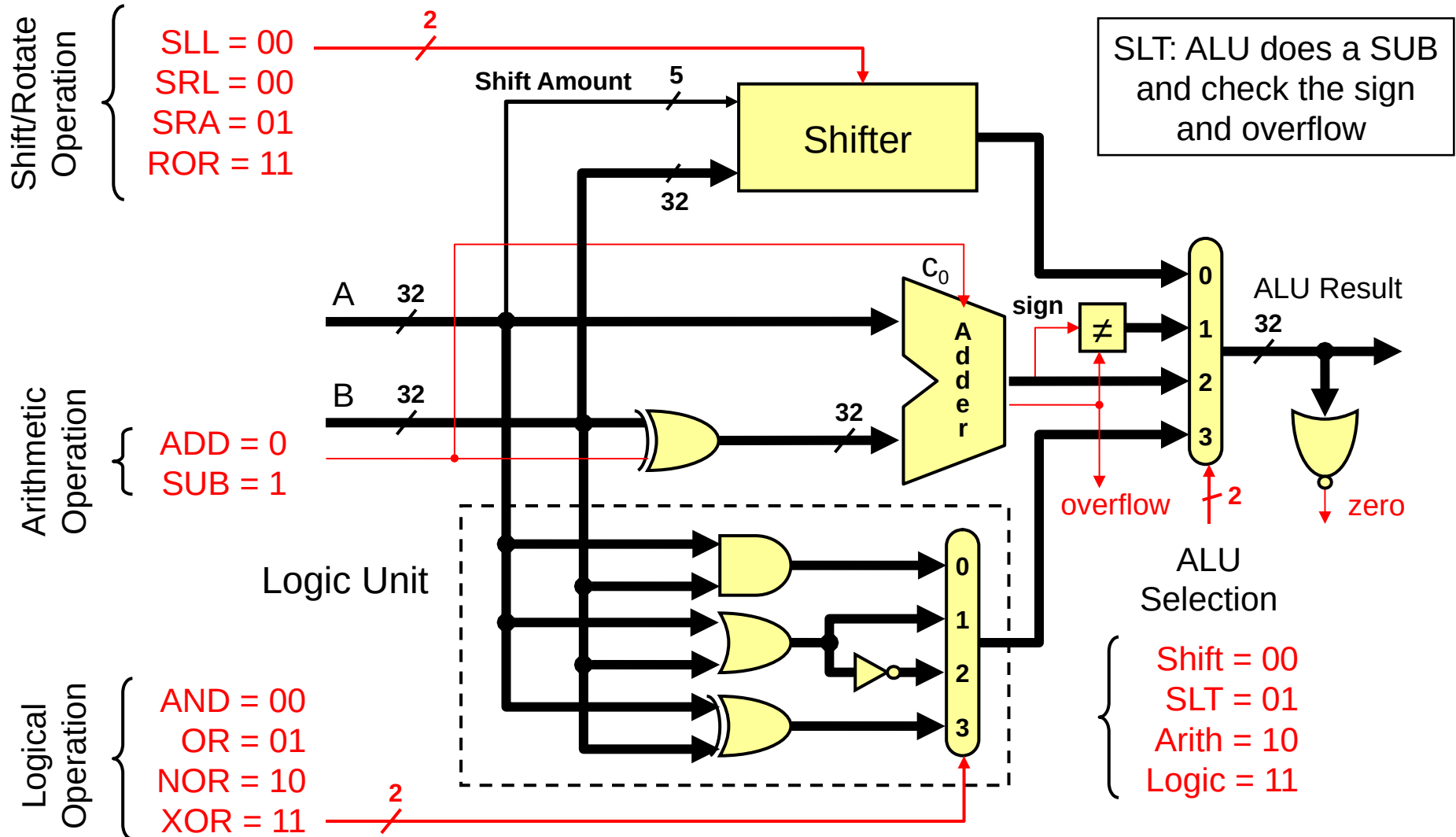

Details of the Shifter

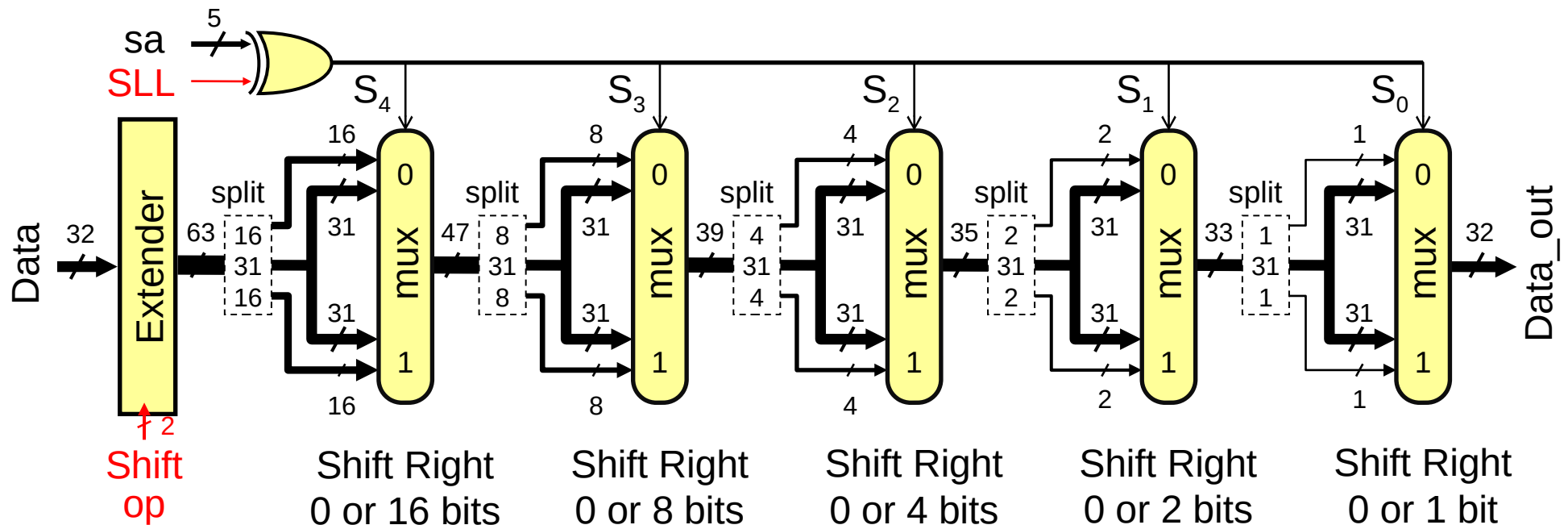- ❖ Implemented with multiplexers and wiring
- ❖ Shift Operation can be: **SLL**, **SRL**, **SRA**, or **ROR**
- ❖ Input Data is extended to 63 bits according to **Shift Op**
- ❖ The 63 bits are shifted right according to $S_4S_3S_2S_1S_0$



Details of the Shifter – cont'd

- ❖ Input data is extended from 32 to 63 bits as follows:
 - ◇ If shift op = SRL then $\text{ext_data}[62:0] = 0^{31} \parallel \text{data}[31:0]$
 - ◇ If shift op = SRA then $\text{ext_data}[62:0] = \text{data}[31]^{31} \parallel \text{data}[31:0]$
 - ◇ If shift op = ROR then $\text{ext_data}[62:0] = \text{data}[30:0] \parallel \text{data}[31:0]$
 - ◇ If shift op = SLL then $\text{ext_data}[62:0] = \text{data}[31:0] \parallel 0^{31}$
- ❖ For SRL, the 32-bit input data is zero-extended to 63 bits
- ❖ For SRA, the 32-bit input data is sign-extended to 63 bits
- ❖ For ROR, 31-bit extension = lower 31 bits of data
- ❖ Then, shift right according to the shift amount
- ❖ As the extended data is shifted right, the upper bits will be: 0 (SRL), sign-bit (SRA), or lower bits of data (ROR)

Implementing Shift Left Logical

- ❖ The wiring of the above shifter dictates a right shift
- ❖ However, we can convert a left shift into a right shift
- ❖ For SLL, 31 zeros are appended to the right of data
 - ◇ To shift left by 0 is equivalent to shifting right by 31
 - ◇ To shift left by 1 is equivalent to shifting right by 30
 - ◇ To shift left by 31 is equivalent to shifting right by 0
 - ◇ Therefore, for SLL use the **1's complement** of the shift amount
- ❖ ROL is equivalent to ROR if we use $(32 - \text{rotate amount})$
- ❖ ROL by 10 bits is equivalent to ROR by $(32 - 10) = 22$ bits
- ❖ Therefore, software can convert ROL to ROR

Instruction and Data Memories

❖ Instruction memory needs only provide read access


- ◇ Because datapath does not write instructions
- ◇ Behaves as combinational logic for read
- ◇ **Address** selects **Instruction** after **access time**

❖ Data Memory is used for load and store

- ◇ **MemRead**: enables output on **Data_out**
 - **Address** selects the word to put on **Data_out**
- ◇ **MemWrite**: enables writing of **Data_in**
 - **Address** selects the memory word to be written
 - The **Clock** synchronizes the write operation


❖ Separate instruction and data memories

 - ◇ Later, we will replace them with **caches**





Clocking Methodology

- ❖ Clocks are needed in a sequential logic to decide when a state element (register) should be updated
- ❖ To ensure correctness, a **clocking methodology** defines when data can be written and read
- ❖ We assume **edge-triggered clocking**
- ❖ All state changes occur on the **same clock edge**
- ❖ Data must be **valid** and **stable** before arrival of clock edge
- ❖ Edge-triggered clocking allows a register to be read and written during same clock cycle

 

Determining the Clock Cycle

 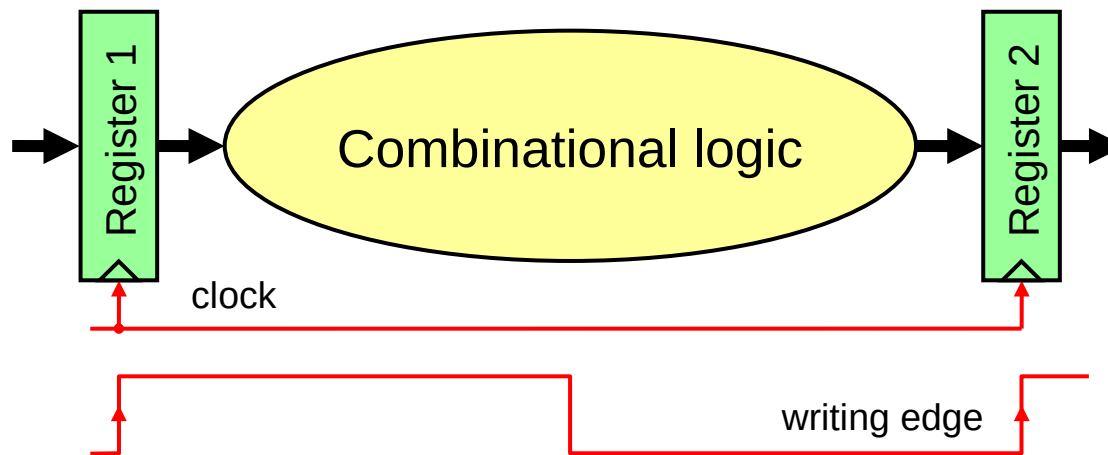- ❖ With edge-triggered clocking, the clock cycle must be long enough to accommodate the path from one register through the combinational logic to another register



$$T_{cycle} \geq T_{clk-q} + T_{max_comb} + T_s$$

- ❖ T_{clk-q} : clock to output delay through register
- ❖ T_{max_comb} : longest delay through combinational logic
- ❖ T_s : setup time that input to a register must be stable before arrival of clock edge
- ❖ T_h : hold time that input to a register must hold after arrival of clock edge
- ❖ Hold time (T_h) is normally satisfied since $T_{clk-q} > T_h$

Clock Skew

- ❖ Clock skew arises because the clock signal uses different paths with slightly different delays to reach state elements
- ❖ Clock skew is the difference in absolute time between when two storage elements see a clock edge
- ❖ With a clock skew, the clock cycle time is increased

$$T_{\text{cycle}} \geq T_{\text{clk-q}} + T_{\text{max_combinational}} + T_{\text{setup}} + T_{\text{skew}}$$


- ❖ Clock skew is reduced by balancing the clock delays

Next . . .

- ❖ Designing a Processor: Step-by-Step
- ❖ Datapath Components and Clocking
- ❖ **Assembling an Adequate Datapath**
- ❖ **Controlling the Execution of Instructions**
- ❖ Main, ALU, and PC Control


Instruction Fetching Datapath

 - ❖ We can now assemble the datapath from its components
- ❖ For instruction fetching, we need ...
 - ◇ Program Counter (PC) register
 - ◇ Instruction Memory
 - ◇ Adder for incrementing PC




The least significant 2 bits of the PC are '00' since PC is a multiple of 4

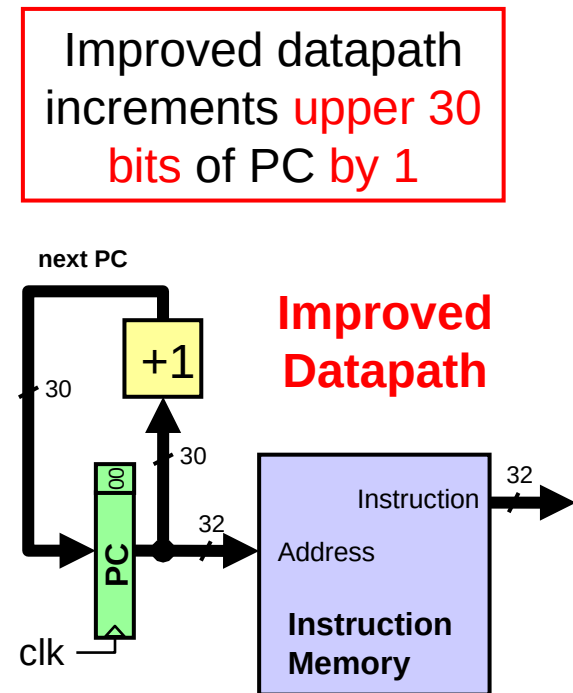Datapath does not handle branch or jump instructions



Datapath for R-type Instructions

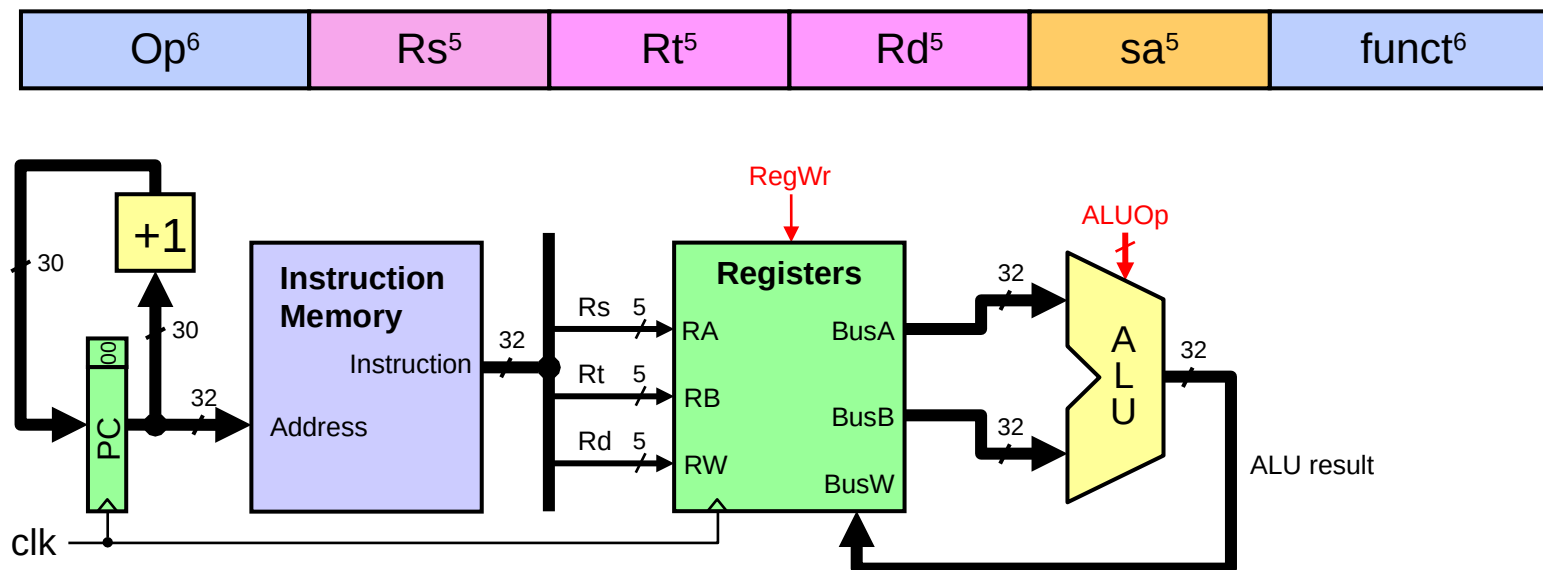

Rs and Rt fields select two registers to read. Rd field selects register to write


BusA & BusB provide data input to ALU. ALU result is connected to BusW

Same clock updates PC and Rd register

❖ Control signals

- ❖ **ALUOp** is the ALU operation as defined in the **funct** field for R-type
- ❖ **RegWr** is used to enable the writing of the ALU result


Datapath for I-type ALU Instructions

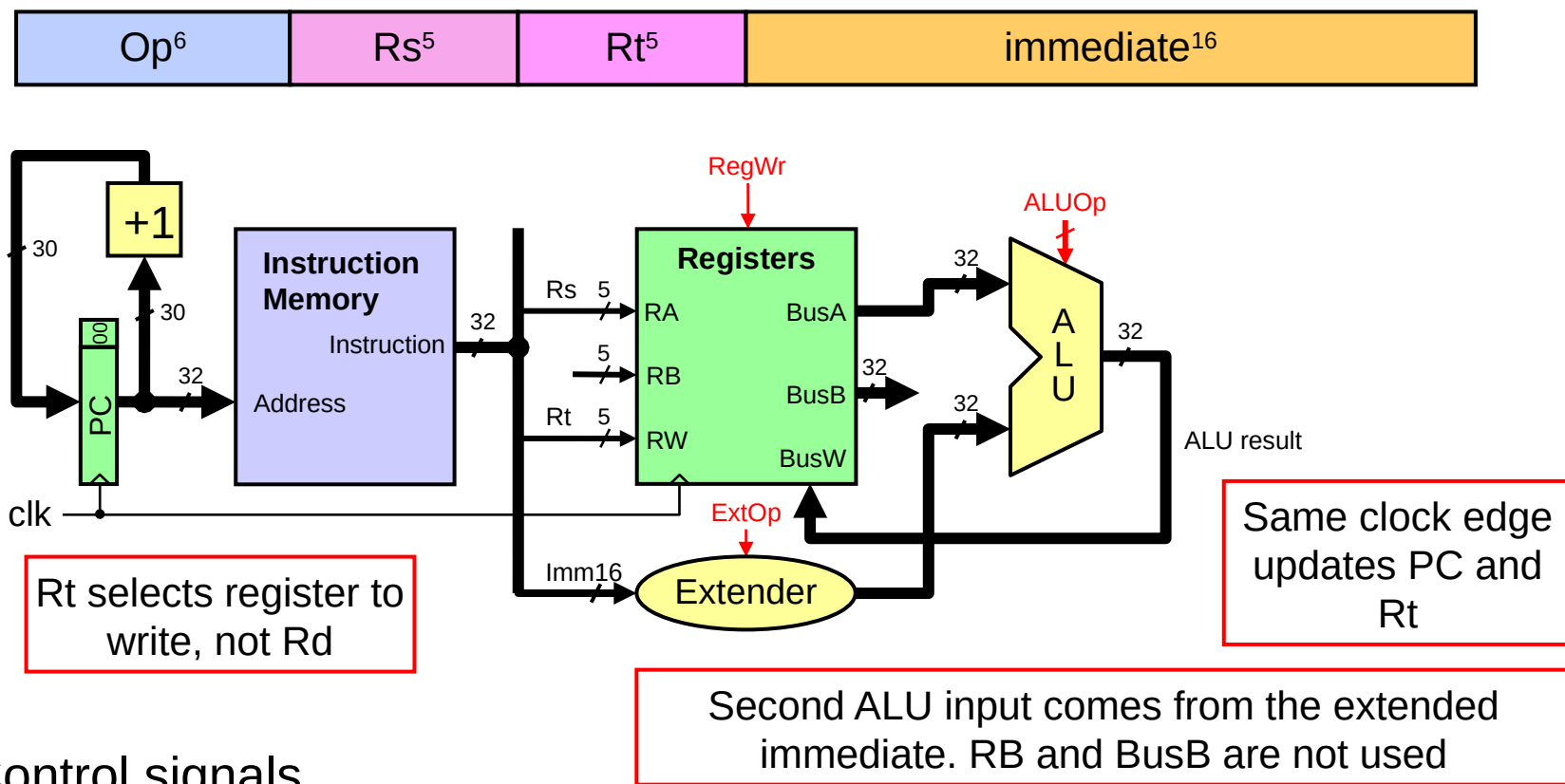

❖ Control signals

- ❖ **ALUOp** is derived from the **Op** field for I-type instructions
- ❖ **RegWr** is used to enable the writing of the **ALU result**
- ❖ **ExtOp** is used to control the extension of the 16-bit immediate

Combining R-type & I-type Datapaths

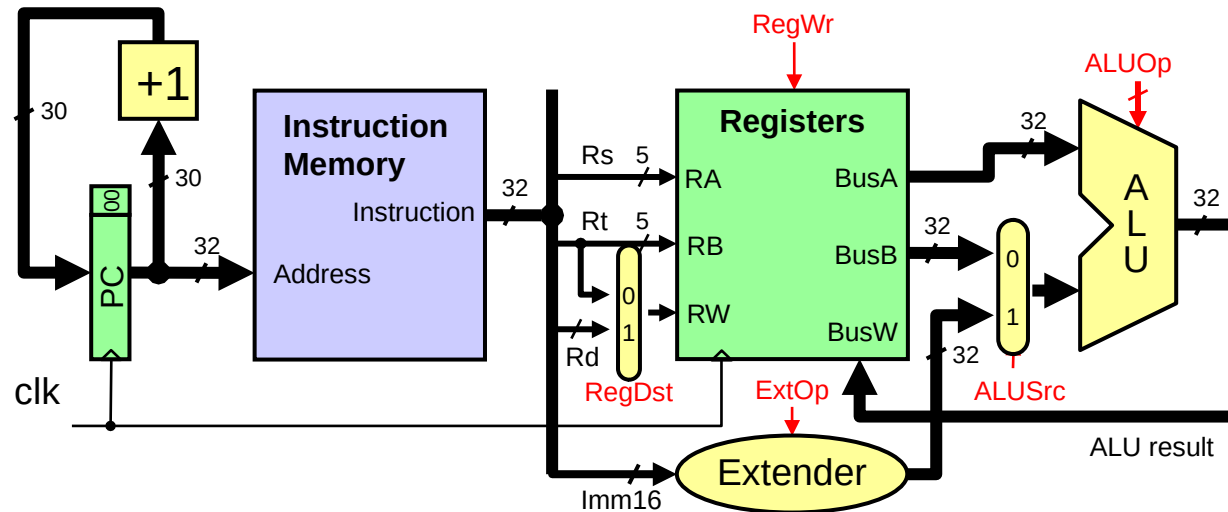


A mux selects RW as either Rt or Rd

Another mux selects 2nd ALU input as either data on BusB or the extended immediate


❖ Control signals

- ❖ **ALUOp** is derived from either the **Op** or the **funct** field
- ❖ **RegWr** enables the writing of the **ALU result**
- ❖ **ExtOp** controls the extension of the 16-bit immediate
- ❖ **RegDst** selects the register destination as either **Rt** or **Rd**
- ❖ **ALUSrc** selects the 2nd ALU source as **BusB** or **extended immediate**

Controlling ALU Instructions

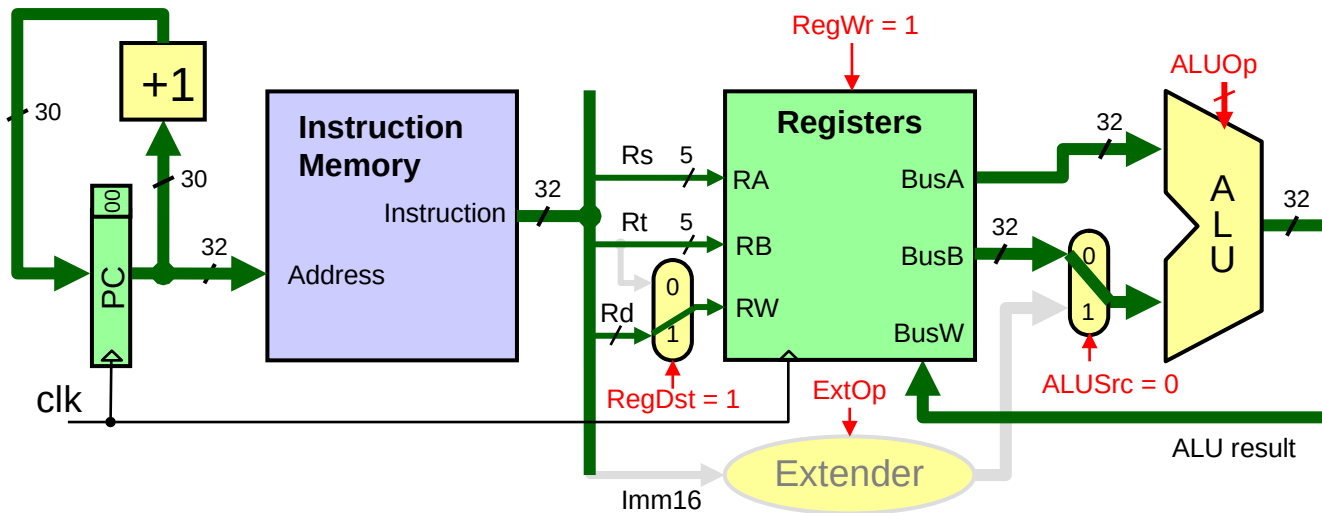


For R-type ALU instructions, **RegDst** is '1' to select Rd on RW and **ALUSrc** is '0' to select BusB as second ALU input. The active part of datapath is shown in **green**

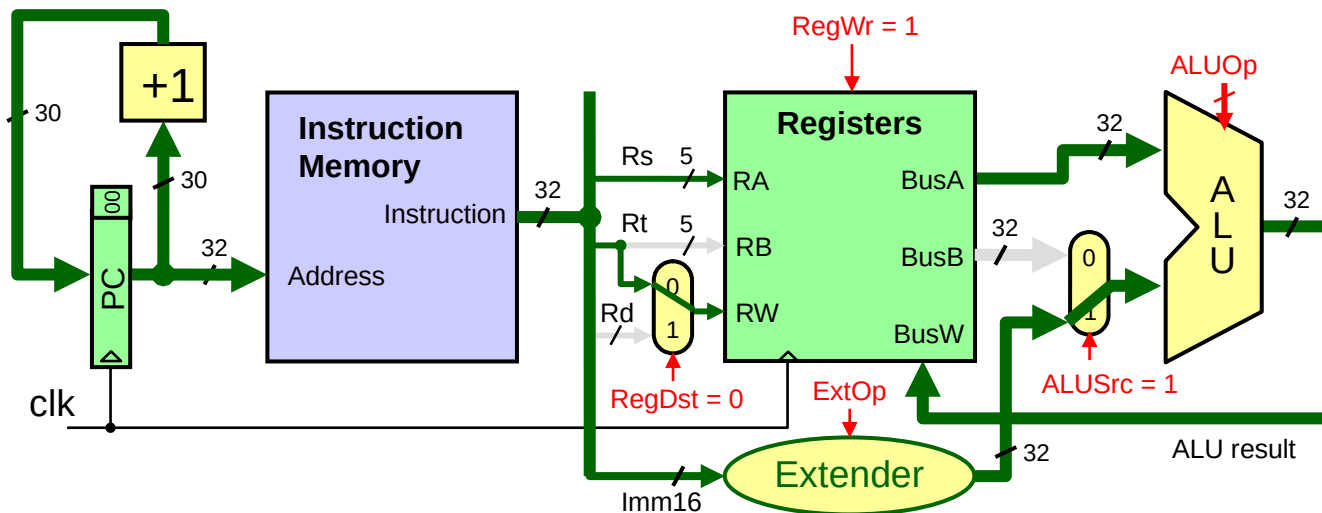

For I-type ALU instructions, **RegDst** is '0' to select Rt on RW and **ALUSrc** is '1' to select Extended immediate as second ALU input. The active part of datapath is shown in **green**


Details of the Extender

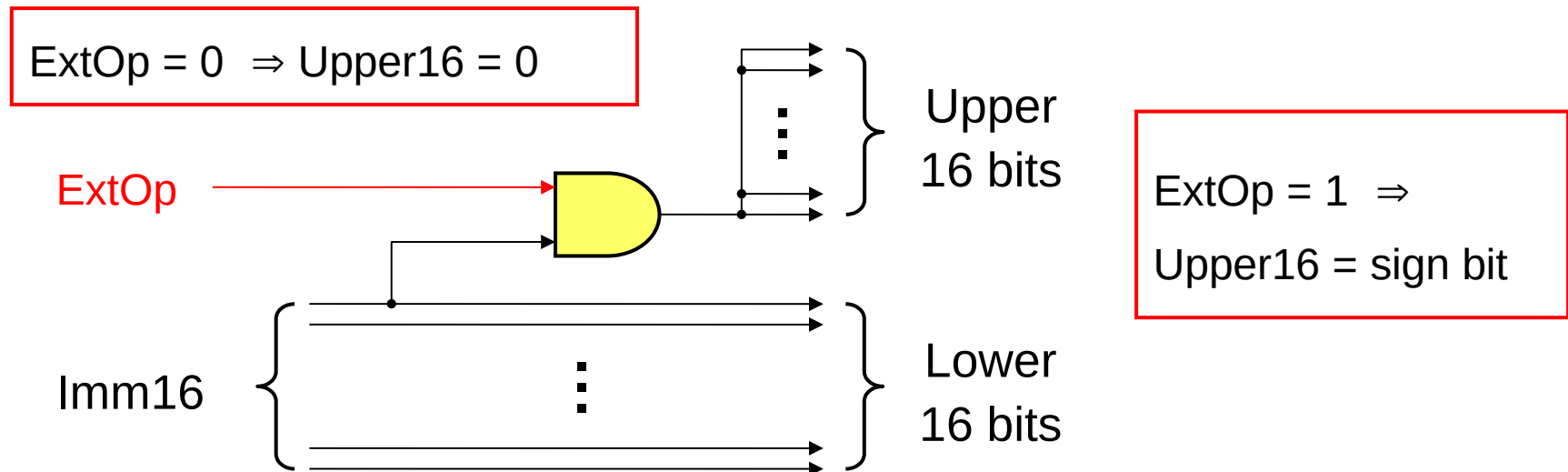- ❖ Two types of extensions
 - ◇ Zero-extension for unsigned constants
 - ◇ Sign-extension for signed constants
- ❖ Control signal **ExtOp** indicates type of extension
- ❖ Extender Implementation: wiring and **one AND** gate



Adding Data Memory to Datapath

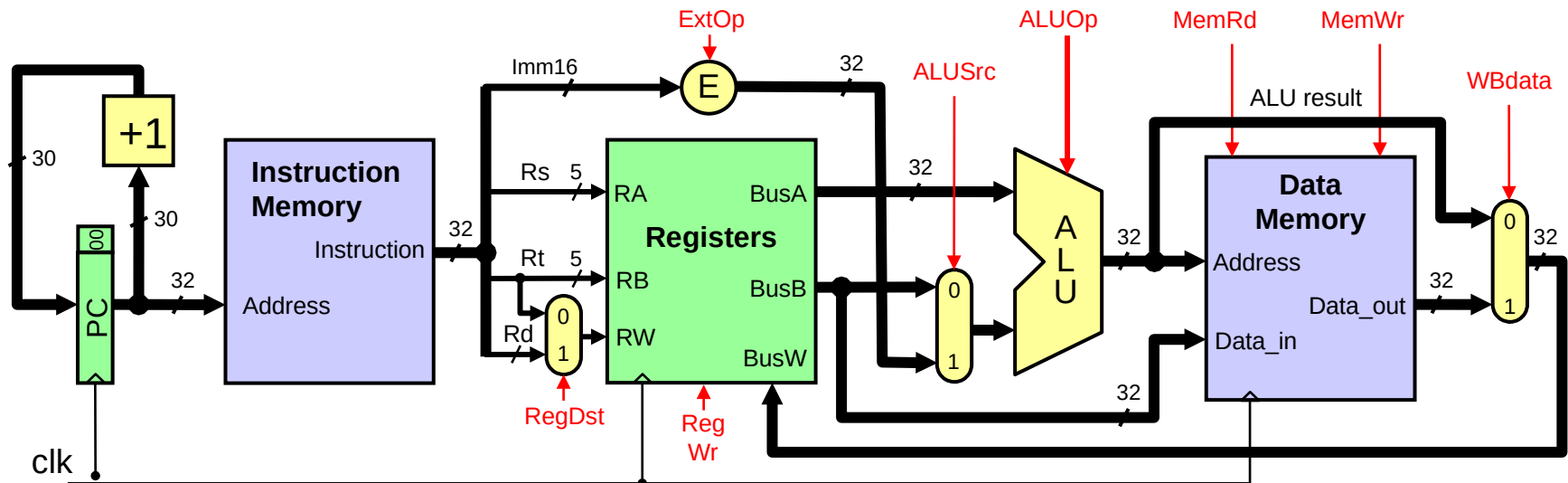- ❖ A **data memory** is added for **load** and **store** instructions



ALU calculates data memory address


A 3rd mux selects data on BusW as either ALU result or memory data_out

- ❖ Additional Control signals

- ◇ **MemRd** for load instructions
- ◇ **MemWr** for store instructions
- ◇ **WBdata** selects data on BusW as **ALU result** or **Memory Data_out**

BusB is connected to Data_in of Data Memory for store instructions

Controlling the Execution of Load

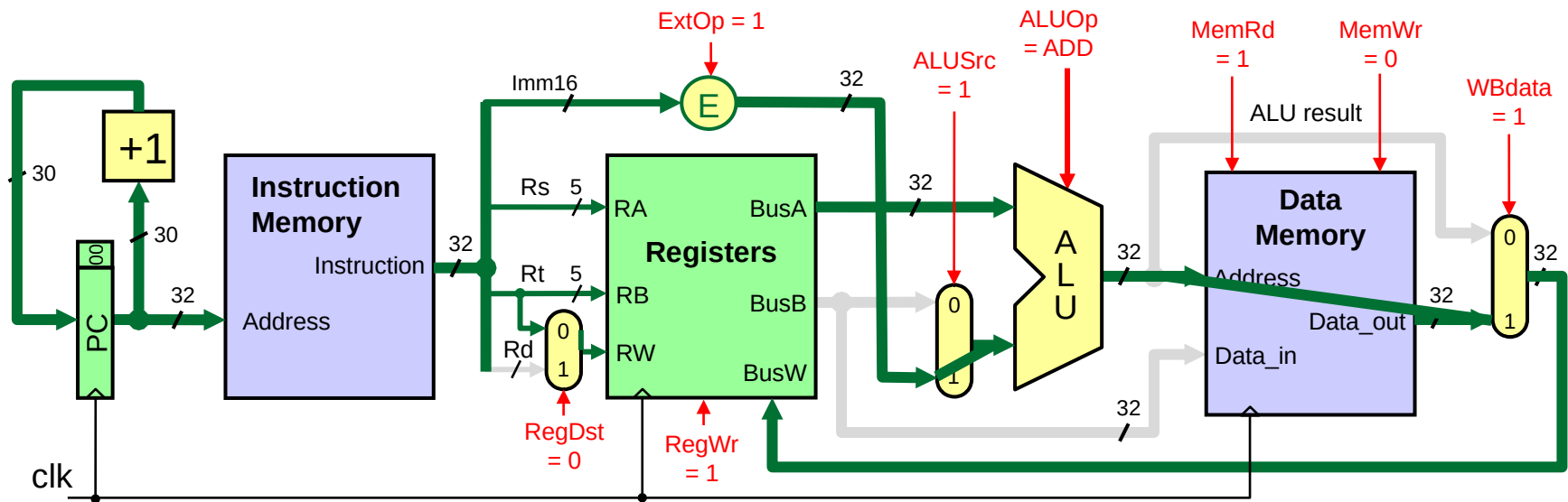

RegDst = '0' selects Rt as destination register

RegWr = '1' to enable writing of register file

ExtOp = 1 to sign-extend Immediate16 to 32 bits

ALUSrc = '1' selects extended immediate as second ALU input


ALUOp = 'ADD' to calculate data memory address as $\text{Reg}(\text{Rs}) + \text{sign-extend}(\text{Imm16})$

MemRd = '1' to read data memory

WBdata = '1' places the data read from memory on BusW

Clock edge updates PC and Register Rt

Controlling the Execution of Store

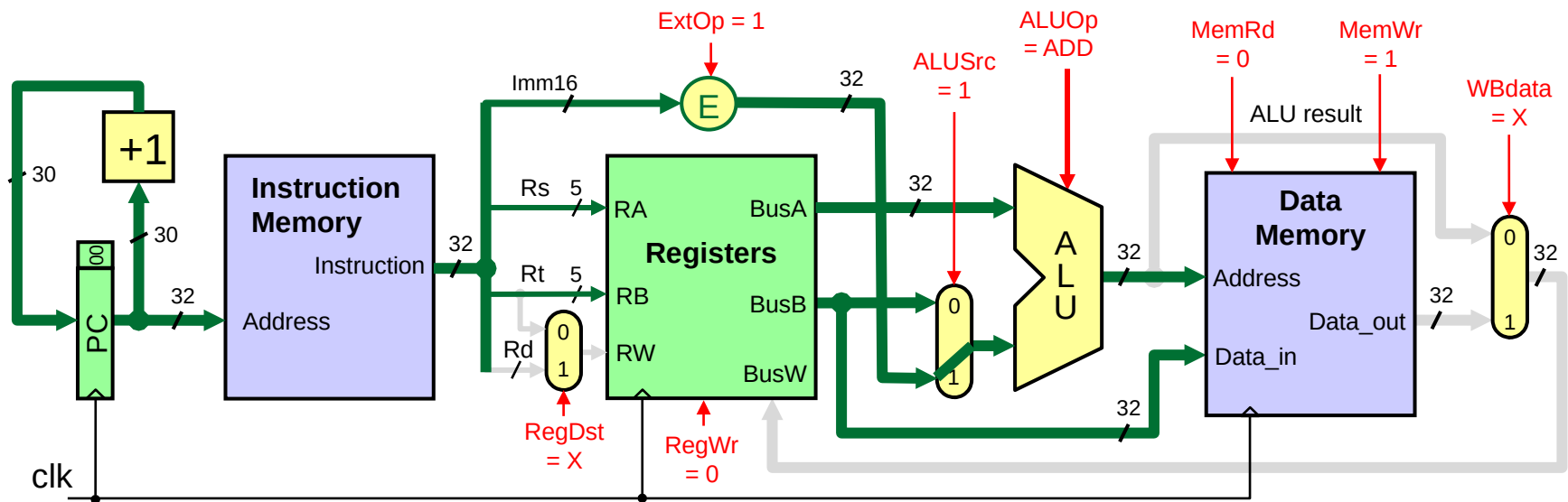

RegDst = 'X' because no register is written

RegWr = '0' to disable writing of register file

ExtOp = 1 to sign-extend Immediate16 to 32 bits

ALUSrc = '1' selects extended immediate as second ALU input


ALUOp = 'ADD' to calculate data memory address as $\text{Reg}(\text{Rs}) + \text{sign-extend}(\text{Imm16})$

MemWr = '1' to write data memory

WBdata = 'X' because don't care what data is put on BusW

Clock edge updates PC and Data Memory


Adding Jump and Branch to Datapath

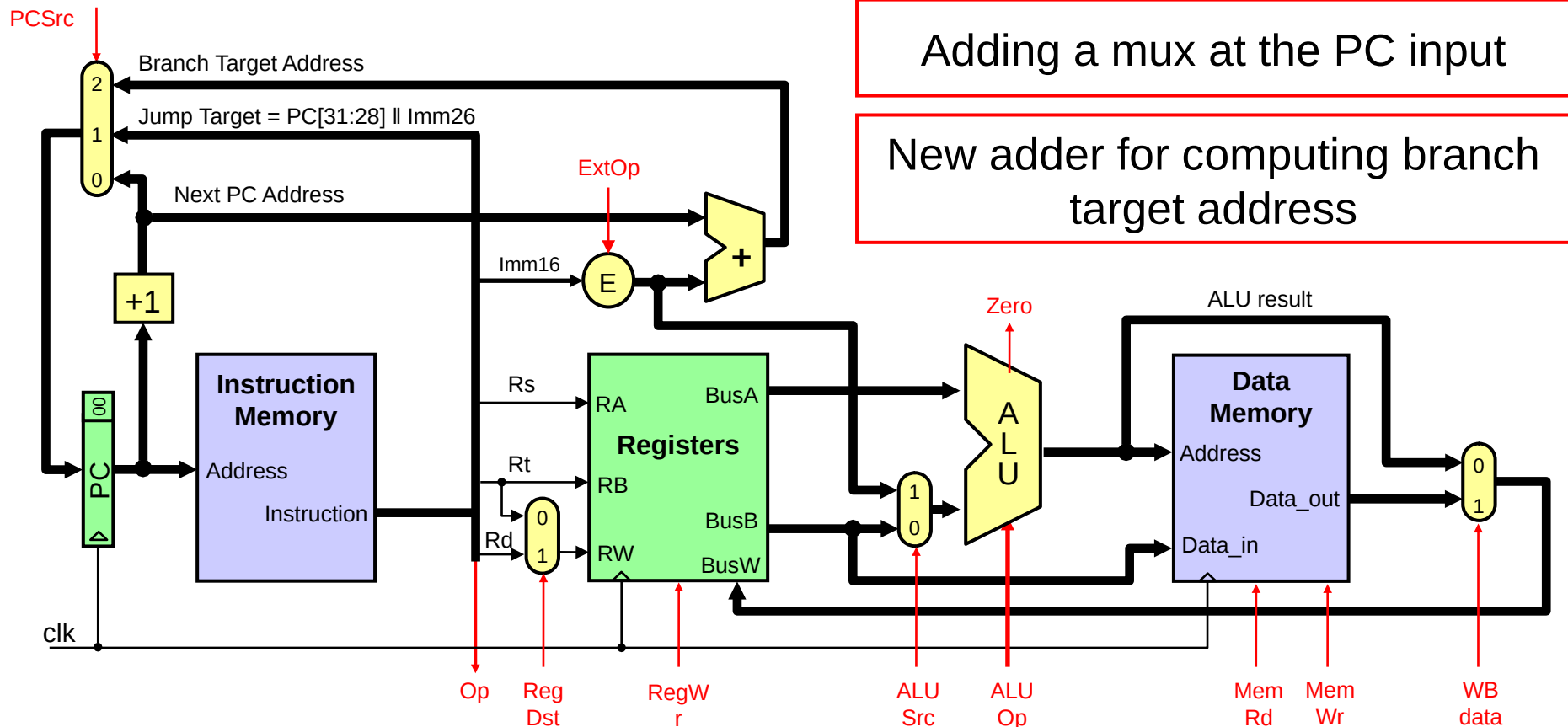

❖ Additional Control Signals

- ❖ **PCSrc** for PC control: **1** for a jump and **2** for a taken branch
- ❖ **Zero** flag for branch control: whether branch is taken or not


Controlling the Execution of a Jump

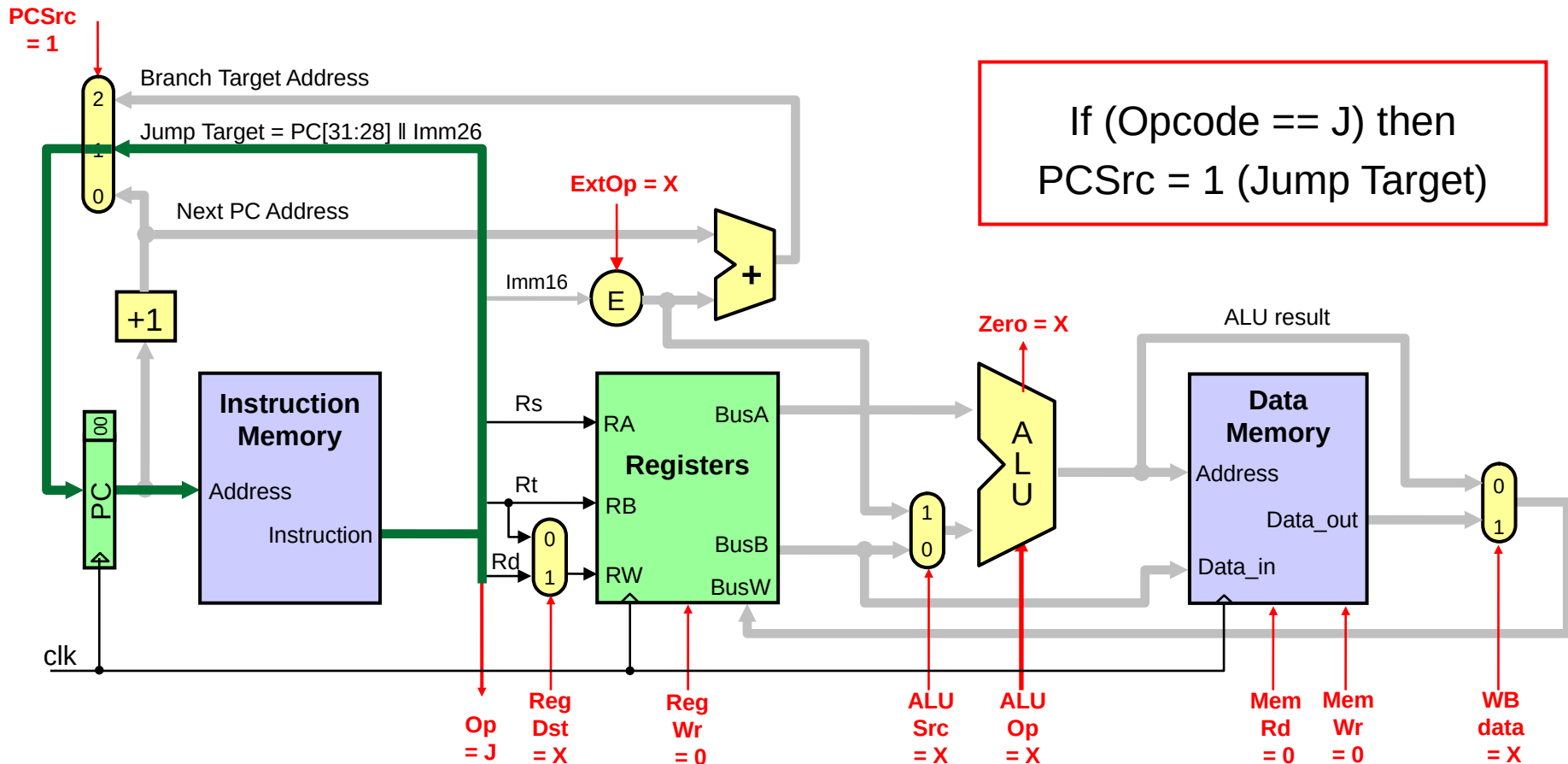

MemRd = MemWr = RegWr = 0, Don't care about other control signals

Clock edge updates PC register only

Controlling the Execution of a Branch

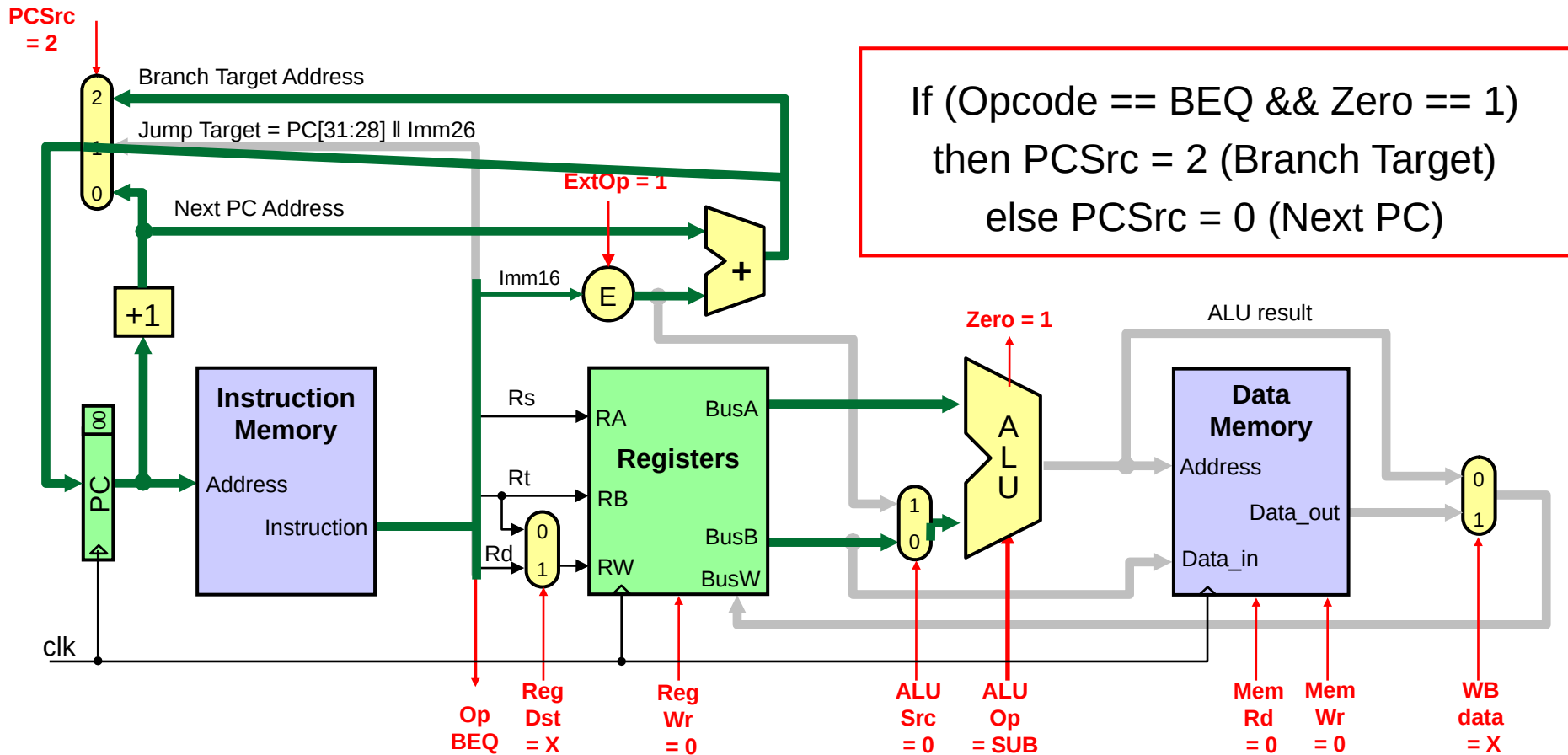

If (Opcode == BEQ && Zero == 1)
then PCSrc = 2 (Branch Target)
else PCSrc = 0 (Next PC)


ALUSrc = 0, ALUOp = SUB, ExtOp = 1, MemRd = MemWr = RegWr = 0

Clock edge updates PC register only


Next . . .

- ❖ Designing a Processor: Step-by-Step
- ❖ Datapath Components and Clocking
- ❖ Assembling an Adequate Datapath
- ❖ Controlling the Execution of Instructions
- ❖ **Main, ALU, and PC Control**

Main, ALU, and PC Control

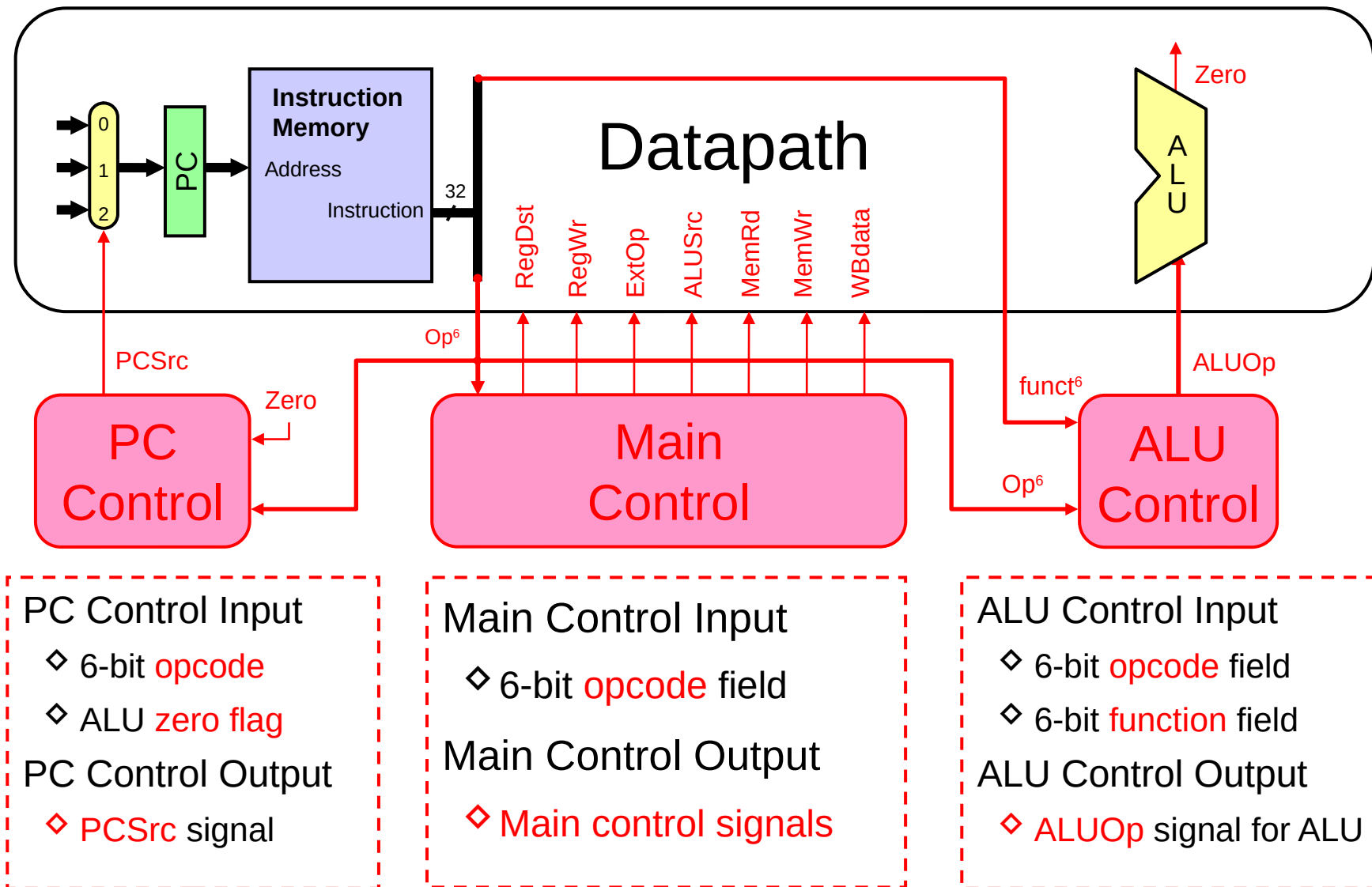

Single-Cycle Datapath + Control

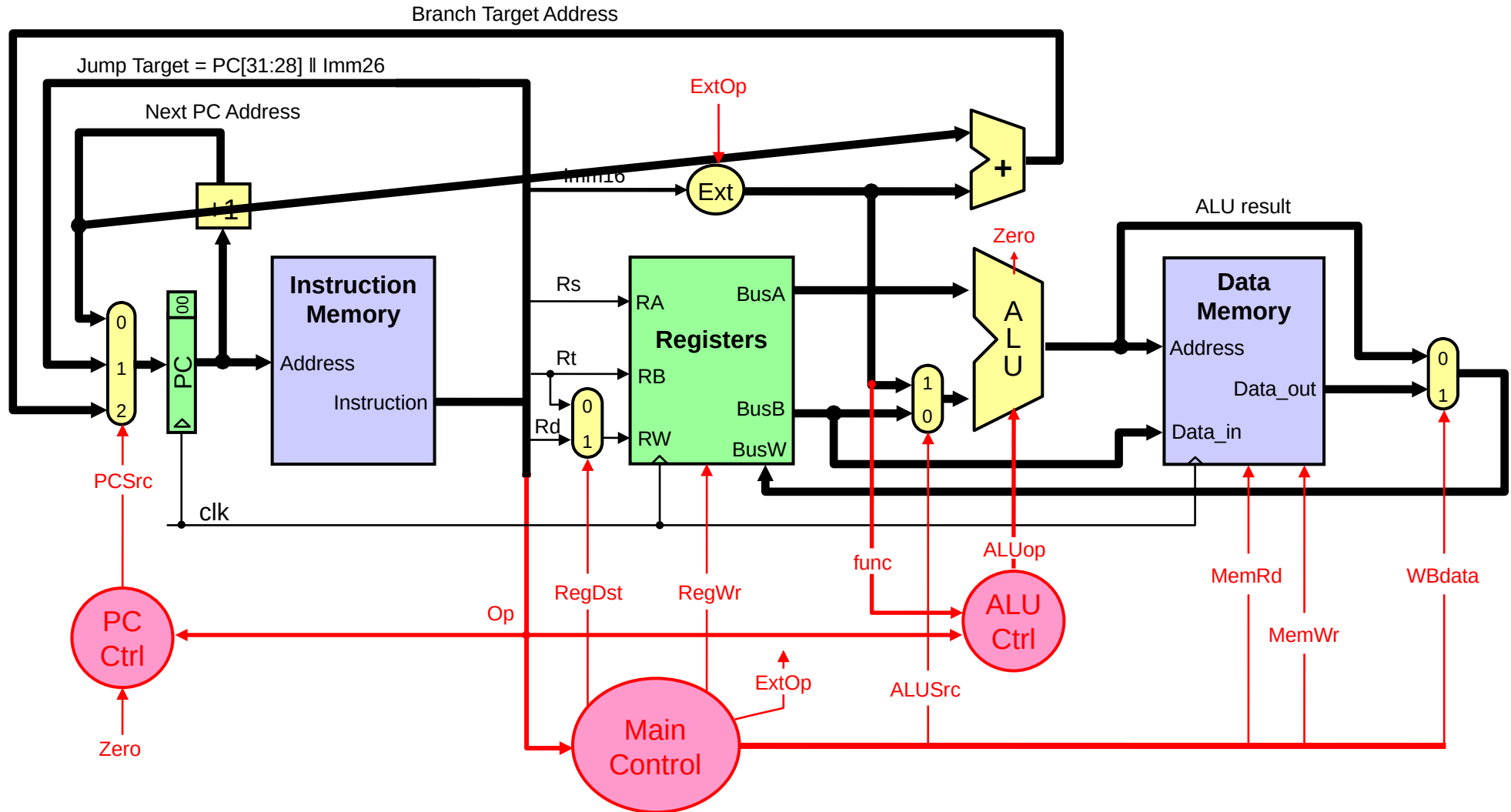

Main Control Signals

Signal	Effect when '0'	Effect when '1'
RegDst	Destination register = Rt	Destination register = Rd
RegWr	No register is written	Destination register (Rt or Rd) is written with the data on BusW
ExtOp	16-bit immediate is zero-extended	16-bit immediate is sign-extended
ALUSrc	Second ALU operand is the value of register Rt that appears on BusB	Second ALU operand is the value of the extended 16-bit immediate
MemRd	Data memory is NOT read	Data memory is read $\text{Data_out} \leftarrow \text{Memory}[\text{address}]$
MemWr	Data Memory is NOT written	Data memory is written $\text{Memory}[\text{address}] \leftarrow \text{Data_in}$
WBdata	BusW = ALU result	BusW = Data_out from Memory

Main Control Truth Table

Op	RegDst	RegWr	ExtOp	ALUSrc	MemRd	MemWr	WBdata
R-type	1 = Rd	1	X	0 = BusB	0	0	0 = ALU
ADDI	0 = Rt	1	1 = sign	1 = Imm	0	0	0 = ALU
SLTI	0 = Rt	1	1 = sign	1 = Imm	0	0	0 = ALU
ANDI	0 = Rt	1	0 = zero	1 = Imm	0	0	0 = ALU
ORI	0 = Rt	1	0 = zero	1 = Imm	0	0	0 = ALU
XORI	0 = Rt	1	0 = zero	1 = Imm	0	0	0 = ALU
LW	0 = Rt	1	1 = sign	1 = Imm	1	0	1 = Mem
SW	X	0	1 = sign	1 = Imm	0	1	X
BEQ	X	0	1 = sign	0 = BusB	0	0	X
BNE	X	0	1 = sign	0 = BusB	0	0	X
J	X	0	X	X	0	0	X

X is a don't care (can be 0 or 1), used to minimize logic

Logic Equations for Main Control Signals

RegDst = R-type

RegWrite = $\frac{(SW + BEQ + BNE + J)}{}$


ExtOp = $\frac{(ANDI + ORI + XORI)}{}$

ALUSrc = (R-type + BEQ + BNE)

MemRd = LW

MemWr = SW

WBdata = LW

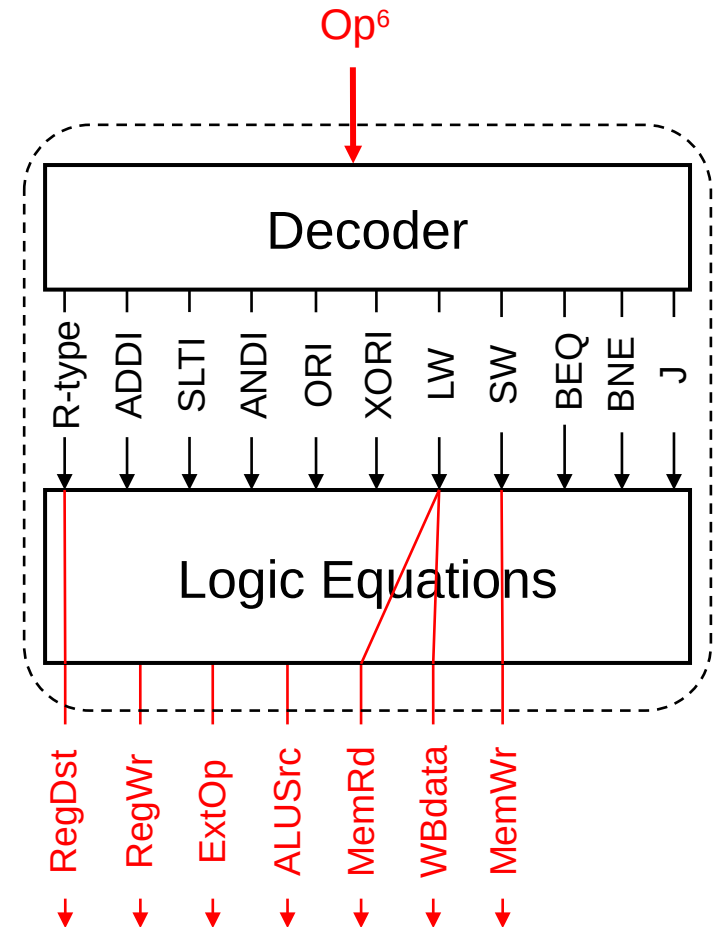

ALU Control Truth Table

Op	funct	ALUOp	4-bit Coding
R-type	AND	AND	0001
R-type	OR	OR	0010
R-type	XOR	XOR	0011
R-type	ADD	ADD	0100
R-type	SUB	SUB	0101
R-type	SLT	SLT	0110
ADDI	X	ADD	0100
SLTI	X	SLT	0110
ANDI	X	AND	0001
ORI	X	OR	0010
XORI	X	XOR	0011
LW	X	ADD	0100
SW	X	ADD	0100
BEQ	X	SUB	0101
BNE	X	SUB	0101
J	X	X	X

The 4-bit Coding defines the binary ALU operations.

Logic equations are derived for the 4-bit coding.

Other bit-coding can be used. The goal is to simplify the ALU control.

PC Control Truth Table


Op	Zero flag	PCSrc
R-type	X	0 = Increment PC
J	X	1 = Jump Target Address
BEQ	0	0 = Increment PC
BEQ	1	2 = Branch Target Address
BNE	0	2 = Branch Target Address
BNE	1	0 = Increment PC
Other than Jump or Branch	X	0 = Increment PC

The ALU Zero flag is used by BEQ and BNE instructions

PC Control Logic

❖ The PC control logic can be described as follows:

```
if (Op == J) PCSrc = 1;  
else if ((Op == BEQ && Zero == 1) ||  
         (Op == BNE && Zero == 0)) PCSrc = 2;  
else PCSrc = 0;
```

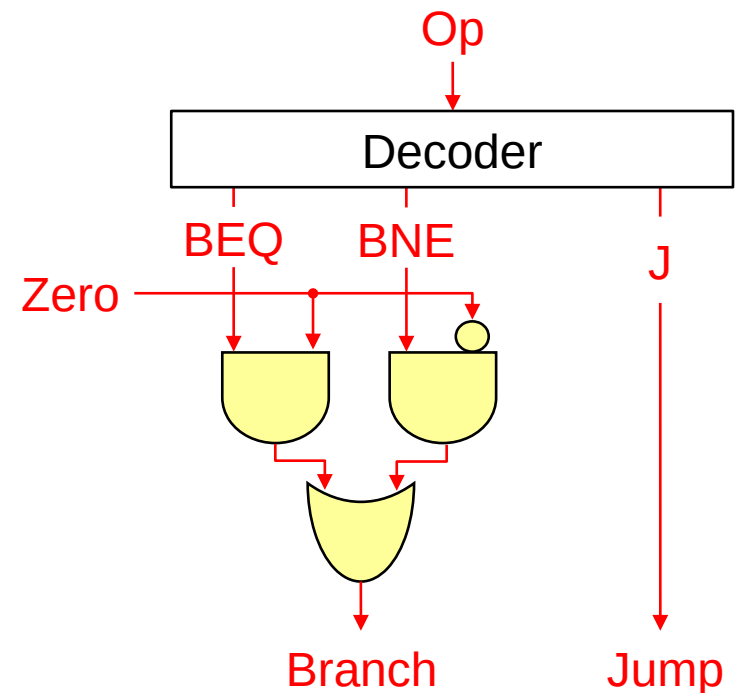

Branch = (BEQ . Zero) + (BNE . Zero)

Branch = 1, Jump = 0  PCSrc = 2

Branch = 0, Jump = 1  PCSrc = 1

Branch = 0, Jump = 0  PCSrc = 0

Summary

❖ 5 steps to design a processor

- ◇ Analyze instruction set => datapath requirements
- ◇ Select datapath components & establish clocking methodology
- ◇ Assemble datapath meeting the requirements
- ◇ Analyze implementation of each instruction to determine control signals
- ◇ Assemble the control logic

❖ MIPS makes Control easier

- ◇ Instructions are of the same size
- ◇ Source registers always in the same place
- ◇ Immediate constants are of same size and same location
- ◇ Operations are always on registers/immediates